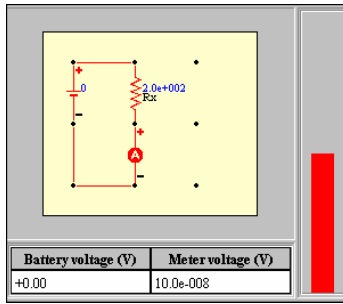



## Worksheet for Exploration 30.5: Voltmeters




A voltmeter measures the voltage across a circuit element and therefore is put in parallel with that element. We can construct a voltmeter by placing a large resistor in series with the galvanometer, which is indicated by  (an ammeter symbol) in the circuit because a galvanometer and an ammeter are essentially the same (see [Exploration 30.4](#)). In this example the galvanometer shows a full-scale indication at a current of  $1 \mu\text{A}$  and the internal resistance of the galvanometer is  $0.2 \Omega$ .

- a. What voltage across the galvanometer produces a full-scale reading?

If we want to measure battery voltages of up to  $2 \text{ V}$ , we'd want the galvanometer needle to give a full-scale indication at this voltage. This means that  $0.2 \mu\text{V}$  must drop across the galvanometer (with a current of  $1 \mu\text{A}$ ) while  $1.9999998 \text{ V}$  must drop across the series resistor. [Restart](#).

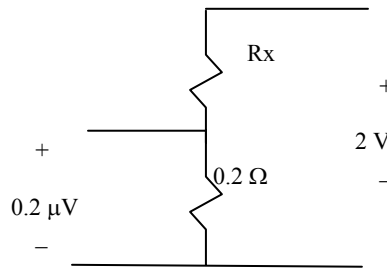- b. Calculate the value of the series resistor required to produce a full scale reading when the input voltage is  $2 \text{ V}$ . Test to see if you get the appropriate reading for a range of battery voltages. (Use the *set values* button.) Specifically, check that, for a battery voltage of  $1 \text{ V}$ , you get a half-scale reading on the indicator bar.



- c. What would the ideal value of internal resistance for a voltmeter be and why?