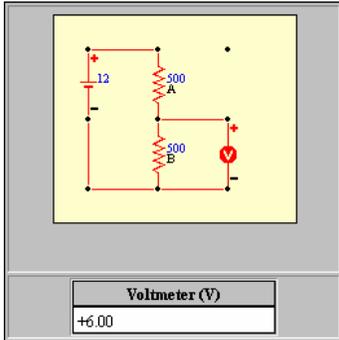


## Worksheet for Exploration 30.3: Designing a Voltage Divider



Often with circuits, not only do you want to be able to figure out what a circuit that is already built is doing, you may want to design a circuit for a specific task. In this case, our task is to design a circuit that is a voltage divider with a particular output voltage (**voltage is given in volts and resistance is given in ohms**). You have a 12-V supply that can give you 1 W of power and you need a 4-V output with as much power as possible. The resistors that you have can dissipate 1 W of power. [Restart](#).

To divide the voltage we can put the power supply in series with two resistors and then use the voltage across one of the resistors to be our 4-V output.

- a. What ratio of resistors do you need to divide the supply voltage by  $1/3$ ? In other words, how many times bigger (or smaller) should resistor A be than resistor B to get an output of 4 V? Try it.

i. Using  $V = IR$ , develop an expression for  $V$  as a function of  $R_A$ ,  $R_B$  and the power supply voltage (12 V).

ii. For an output voltage of 4 V, what is the equation that relates  $R_A$  and  $R_B$ .

iii. Try it:  $R_A =$  \_\_\_\_\_  $R_B =$  \_\_\_\_\_.

- b. Once the ratio is set up, do you have the maximum available power? To determine this, figure out the power used from the voltage source ( $P = VI$ ). To get the maximum power (at a fixed voltage), should you increase or decrease the resistance in the circuit?

P from the power supply = \_\_\_\_\_.

- i. If you increase the total resistance in the circuit, will the power dissipated by the circuit increase or decrease? Explain.

c. What is the limit on the total resistance ( $R_A + R_B$ ) and, therefore, the limit on each resistor. Try it.

i. What is the value of the current,  $I$ , for the maximum power from the power supply?

ii. What then, is the limit on the total resistance and the total resistance for each resistor?

d. Try using a smaller value of resistance. Does the power supply burn up? (Fortunately, you can simply restart the animation and try again).

e. Double the values of  $R_A$  and  $R_B$ . How much power does this circuit now draw from the battery?

Now that you have determined convenient values of  $R_A$  and  $R_B$  that produce a 4-Volt output, replace the voltmeter with a [light bulb](#). (Adding a power consuming circuit element is sometimes referred to as adding a "load.")

f. When this light bulb is added, what is the voltage across the light bulb?

g. Why is it less than 4 V?

(Hint: Think about the current going through the light bulb.)

h. If you increase  $R_A$  and  $R_B$  more, what happens to the voltage across the light bulb? Why? This is the reason voltage dividers like this are made from resistors that are as small as possible.