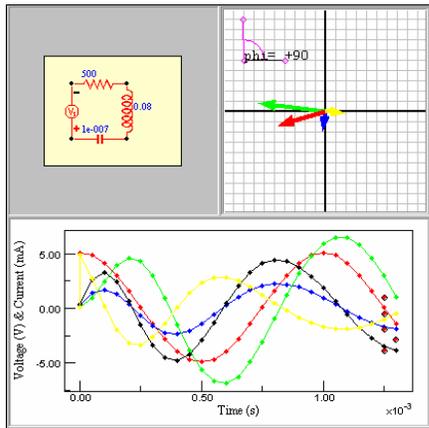


Worksheet for Exploration 31.6: RLC Circuits and Phasors



Assume an ideal power supply. The graph shows the voltage as a function of time across the source (**red**), the resistor (**blue**), the capacitor (**green**) and the inductor (**yellow**), as well as the current through the circuit (**black**) (voltage is given in volts, current is given in milliamperes, angles are given in degrees, and time is given in seconds). [Restart](#).

From the vectors on the phasor diagram, we can develop a connection between the peak (or rms) voltage and the peak (or rms) current, where $V_0 = I_0 Z$ and the phase difference between the voltage and current is given by ϕ . On the phasor diagram, V_0 (**the source voltage-red**) is the vector sum of the three voltage vectors (**resistor-blue**, **inductor-yellow** and **capacitor-green**) and ϕ is the angle between V_0 and the resistor phasor (since resistor current and voltage are in phase). The y components of the phasor vectors are the voltages across the various circuit elements. See [Illustrations 31.6](#) and [31.7](#) as well as [Exploration 31.5](#).

- Explain the phase difference between the blue, yellow and green vectors in the phasor animation.
- Pick a frequency and pause the animation. Verify that the red vector is the vector sum of the other three vectors.
- Pick a frequency and measure ϕ on the phasor diagram using the pink protractor.

Frequency = _____

i. Current phasor is in phase with the resistor voltage phasor. Why?

ii. Phase shift (angle between current (resistor voltage) and source voltage) = _____

- Explain how you can tell that the phasor animation matches the voltage and current versus time graph for the circuit.

- e. Also measure the phase angle on the voltage and current graphs. To measure the phase angle, since one period ($1/f$) represents a phase shift of 2π , measure the time difference between the peaks of the voltage and current plots and divide by the period.

T (period) = _____

t_1 = Time at a maximum of voltage = _____

t_2 = Time at nearest maximum of current = _____

ϕ = phase shift = $2\pi(t_1 - t_2)/T$ = _____

- f. Measure Z for this same frequency ($Z = V_0 / I_0$). Check your answers by using the equations for impedance and the phase shift between the voltage and the current, $Z = (R^2 + (\omega L - 1/\omega C)^2)^{1/2}$ and $\cos\phi = R / Z$.

Frequency = _____

V_{rms} = _____ I_{rms} = _____

$Z = V_0 / I_0 = V_{\text{rms}} / I_{\text{rms}} =$ _____

Comparison with $R \cos \phi =$ _____

and $(R^2 + (\omega L - 1/\omega C)^2)^{1/2} =$ _____